

Answers to Chapter 3 questions

Activity 3.1

Input values		Value	Value	Output	Value	Value	Output
A	B	$(a \cdot \bar{b})$	$(\bar{a} \cdot b)$	+	$(a + b)$	$(\bar{a} \cdot \bar{b})$.
0	0	0	0	0	0	1	0
0	1	0	1	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	0	1	0	0

Both truth tables have the same output (columns 5 and 8). Hence both expressions are the same.

Activity 3.2

a

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

b

Inputs		Output
A	B	X
0	0	0
0	1	0
1	0	0
1	1	0

c

Inputs			Output
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


d

Inputs			Output
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


e

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Activity 3.3

 
a $X = 1$ if $(A = 1 \text{ OR } B = 1) \text{ OR } (A = 0 \text{ AND } B = 1)$ 

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

 b $Y = 1$ if $(A = 0 \text{ AND } B = 0) \text{ AND } (B = 0 \text{ OR } C = 1)$ 


Inputs			Output
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 c $T = 1$ if $(K = 1 \text{ OR } L = 1) \text{ OR } (K = 1 \text{ AND } M = \text{NOT } 1) \text{ OR } (M = 1)$




Inputs			Output
K	L	M	T
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 d $x = (a \cdot \bar{b}) + (\bar{b} \cdot c)$



Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 
e $R = 1$ if $(A = 1 \text{ AND } B = 1) \text{ AND } (B = 1 \text{ OR } C = \text{NOT } 1)$



Inputs			Output
A	B	C	R
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Activity 3.4

 a $X = 1$ if $(R = \text{NOT } 1) \text{ OR } (C = 1 \text{ AND } T = \text{NOT } 1) \text{ OR } (R = 1 \text{ AND } T = \text{NOT } 1)$



Inputs			Output
R	T	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 b $S = 1$ if $(G = 1 \text{ AND } W = \text{NOT } 1) \text{ OR } (G = \text{NOT } 1 \text{ AND } R = 1) \text{ OR } (W = 1 \text{ AND } R = 1)$



Inputs			Output
G	R	W	S
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Activity 3.5

First logic circuit:

Inputs		Output
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

which confirms this as an AND gate.

Second logic circuit:

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

which confirms this as an OR gate.


Third logic circuit:

Input	Output
A	X
0	1
1	0

which confirms this as a NOT gate.

Activity 3.6


a

 

Inputs			Output from original circuit	Output from NAND gate only circuit
A	B	C		
0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

which confirms that the two logic circuits have the same function.

b NAND-gate only circuit:

 

c This gives the following truth table:

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

which confirms that the logic circuit represents the XOR gate.

Activity 3.7

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

which is the truth table for the NOR gate.

Activity 3.8

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

which is the truth table for the NOR gate.

Activity 3.9

Inputs			Output
P	Q	R	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

which indicates that the logic circuit could be replaced by Input R only.